 


Current Foldback for Type 2 PSE

Thong Huynh
Maxim Integrated Products




Current Foldback for Type 2 PSE

- **Design Targets:**


- Keep PSE switch (MOSFET) power dissipation to within its SOA
- Allows PSE to sustain port power (at reduced current) during transient over load condition

- **PSE Requirements:**

- PSE port voltage range: 50V – 57V
- PSE $I_{port_MAX} = 720\text{mA}$ at 50V
- PSE $I_{lim_MAX} = 720\text{mA} \times 400/350 = 823\text{mA}$ at 50V
 - PSE must provide at least 823mA at $V_{port} = 50\text{V}$
 - PSE can reduce its current limit (foldback) when $V_{port} < 50\text{V}$
 - To control precisely the power dissipation in the MOSFET, it's better to specified the current limit foldback as a function of V_{ds} .

 

Current Foldback for Type 2 PSE

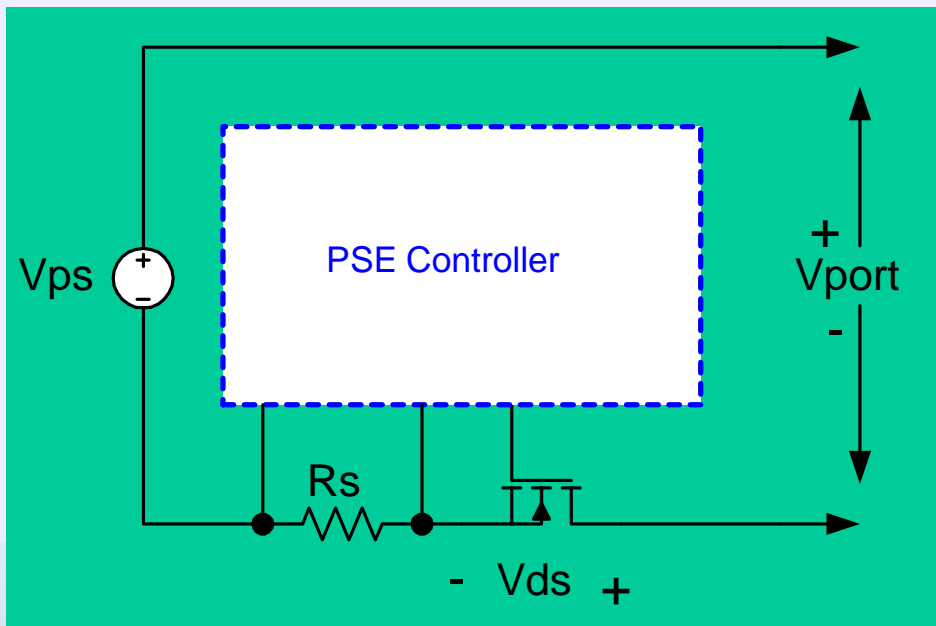


$$V_{ds} = V_{ps} - V_{port}$$

(neglect voltage drop across R_s)

$$V_{ps} = 57V \text{ maximum}$$


$$V_{port} = 50V \text{ minimum}$$

 → $V_{ds} = 57V - 50V = 7V$
minimum before the
controller can start
folding back






 
Maximum Safe Operation Area – 100V, 120mΩ MOSFET



 
This is roughly a constant power curve which limit this MOSFET power dissipation to ~30W for 75ms




Current Foldback for Type 2 PSE

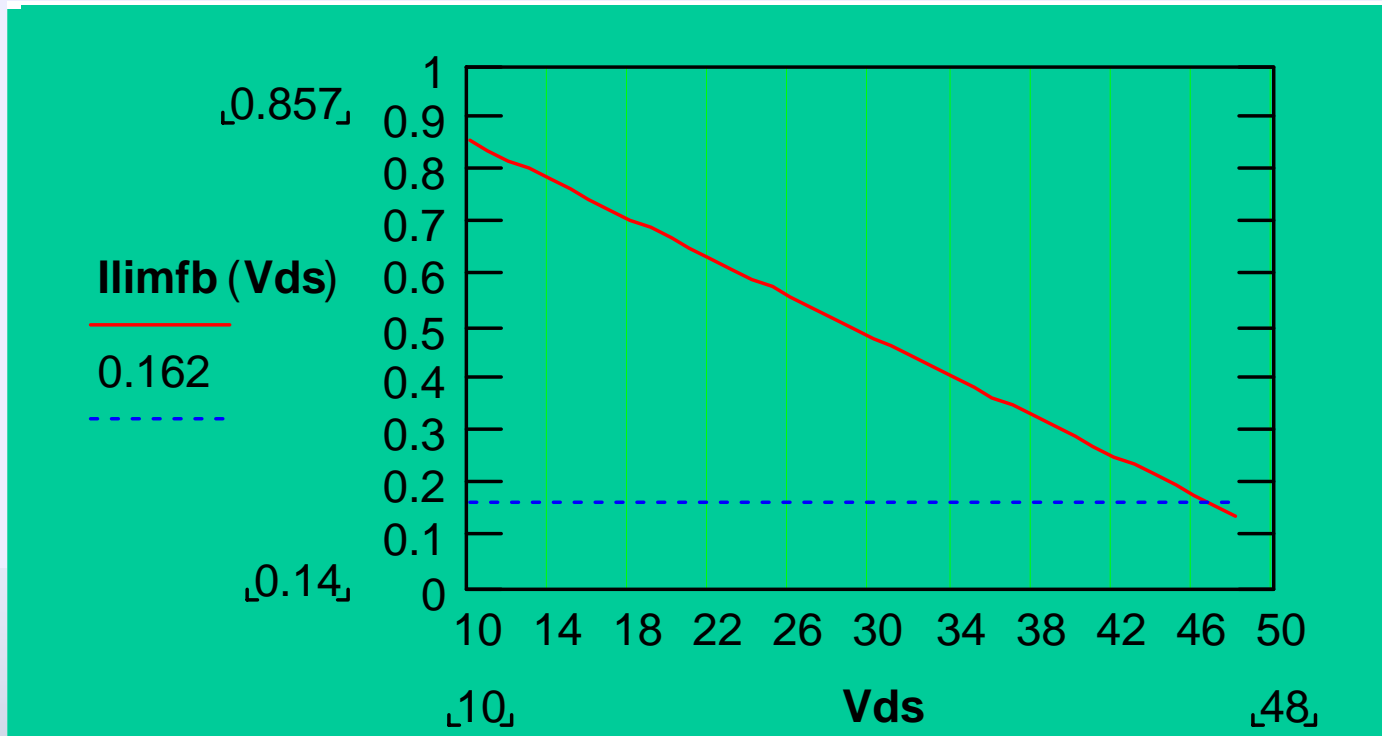

 
Example: PSE current limit as a linear function of V_{ds}



Current Foldback for Type 2 PSE

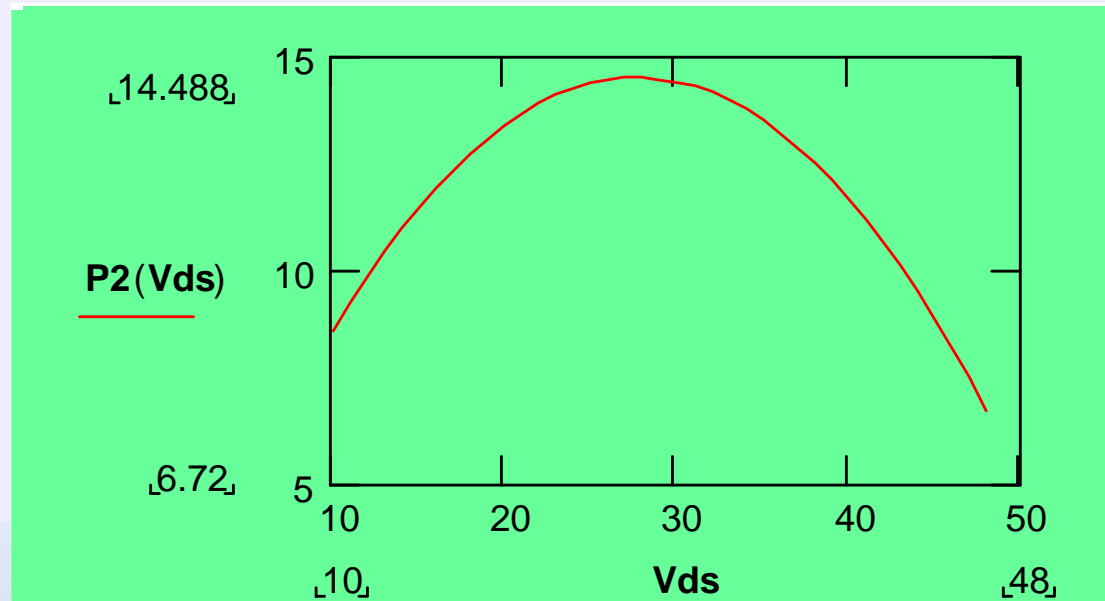

 MOSFET power dissipation as a function of V_{ds} . Peak power dissipation is 14.5W at $V_{ds} = 28V$



Current Foldback for Type 2 PSE

- **Summary:**
 - In a type 2 PSE, A simple current foldback implementation can help maintain the PSE MOSFET in its safe operating area.
 - Current foldback allows the PSE to sustain port power during transient condition.

