

# Complexity and Integration of TDD-based PHY at the Camera Side

March 10, 2025  
Atlanta, Georgia

Ahmad Chini, Mehmet Tazebay  
Broadcom Corporation

## Contributors


- Kambiz Vakilian, Broadcom Corporation

# Foreword

- A TDD-based PHY design was proposed for 802.3dm camera Link<sup>1</sup>. The TDD reverse link runs at 3Gsp/s with PAM2 modulation and ~6% duty cycle (effective bit rate of 100Mbps).
- A camera side equalizer with 6-tap DFE was verified in simulations to provide better than 30dB decision point SNR for a typical link segment . The simulation includes PoC filter distortion, link segments with multiple inline connectors and assumes a noise floor of -145dBm/Hz.
- The implementation complexity (area) and power is estimated for the 3Gsp/s Camera side transceiver in this presentation.
- A comparison with incumbent discrete PHY implementations and integration with image sensors is discussed for multiple technology node sizes.



1- [https://www.ieee802.org/3/dm/public/0125/Chini\\_3dm\\_01a\\_0125.pdf](https://www.ieee802.org/3/dm/public/0125/Chini_3dm_01a_0125.pdf)

# 3GspS Equalizer

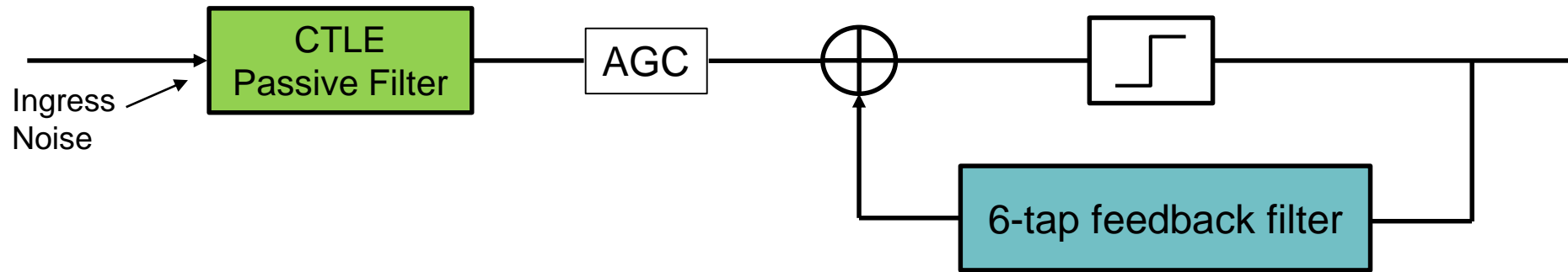



- The CTLE is a passive filter and not adapted to the cable length (high pass and low pass).
- The feedback filter is adapted to the cable length using sign-LMS algorithm.
- The adaptation is performed once every 8 symbols at 375MHz. After initial adaptation, the filter updates may be reduced to periods longer than 1ms.
- Given no FFE taps used and baud rate is 3GspS, the transceiver can be implemented with a mixed mode technology and feedback filter without unrolling the DFE taps.
- The power consumed in the 6-tap filter is mostly scaled with the baud rate and it drops during the reverse link silent periods.
- The same equalizer type can operate in both sides of the link when operating at 2.5Gbps/100Mbps mode.

# Simulation results: Link Segment of 3m

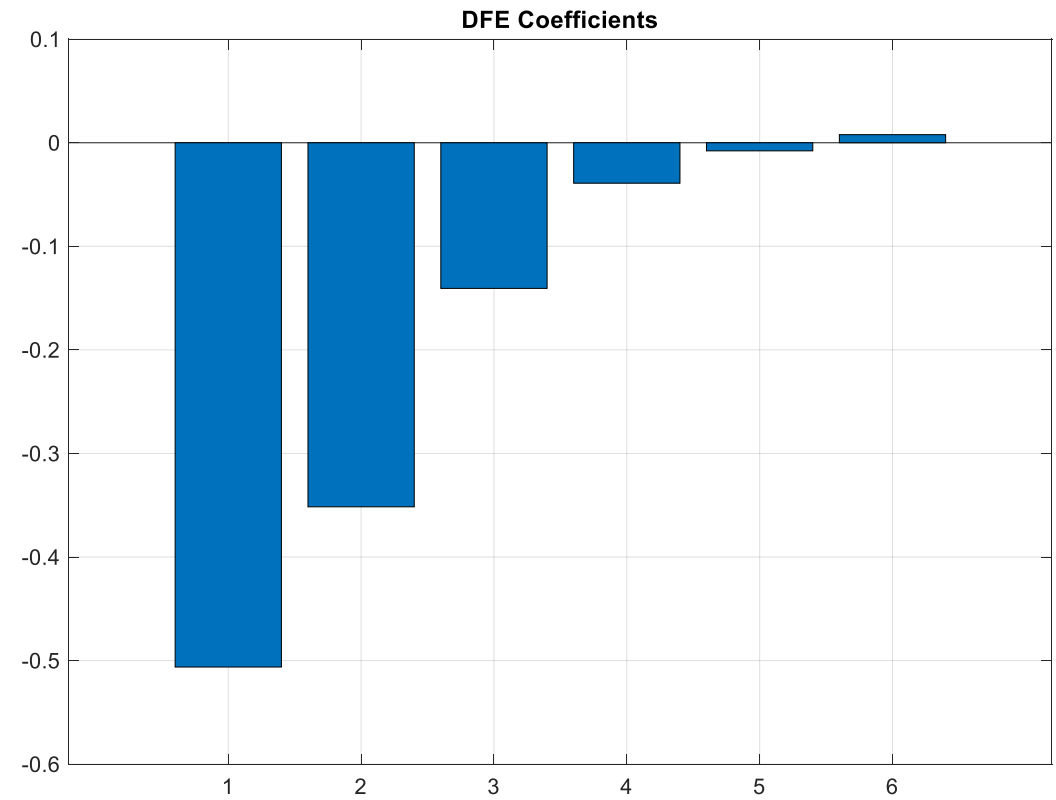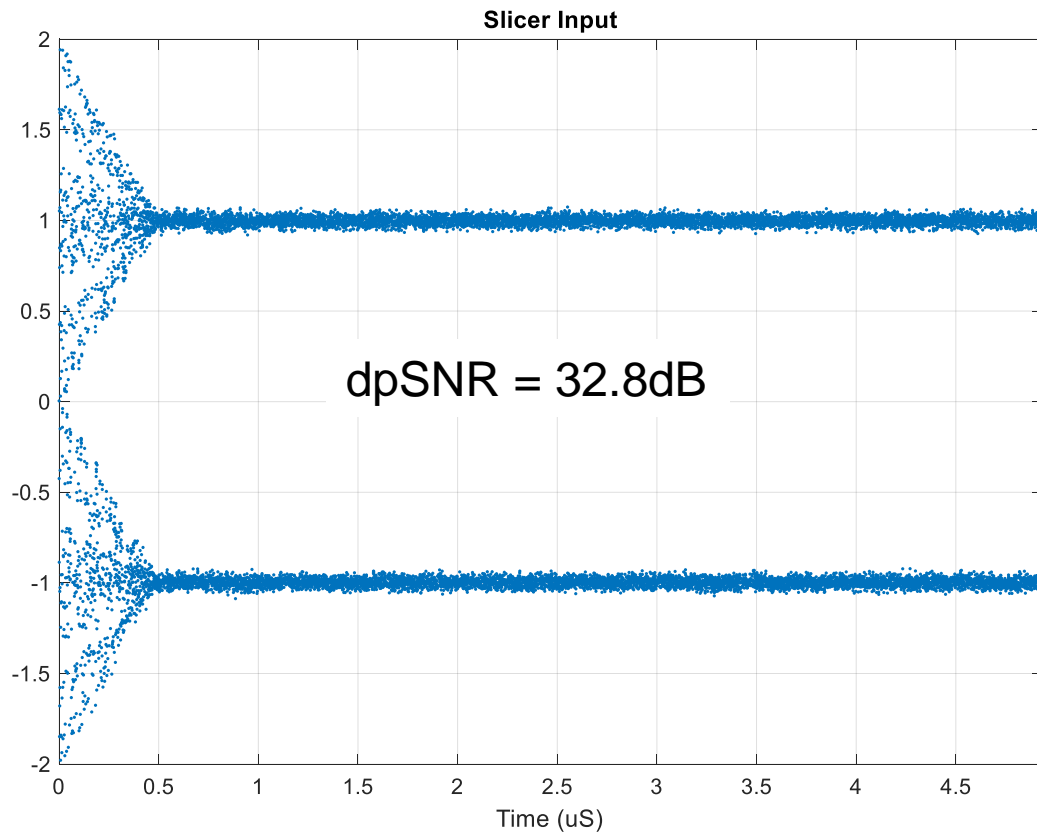



- The Link Segment is a 3m cable with no inline connector
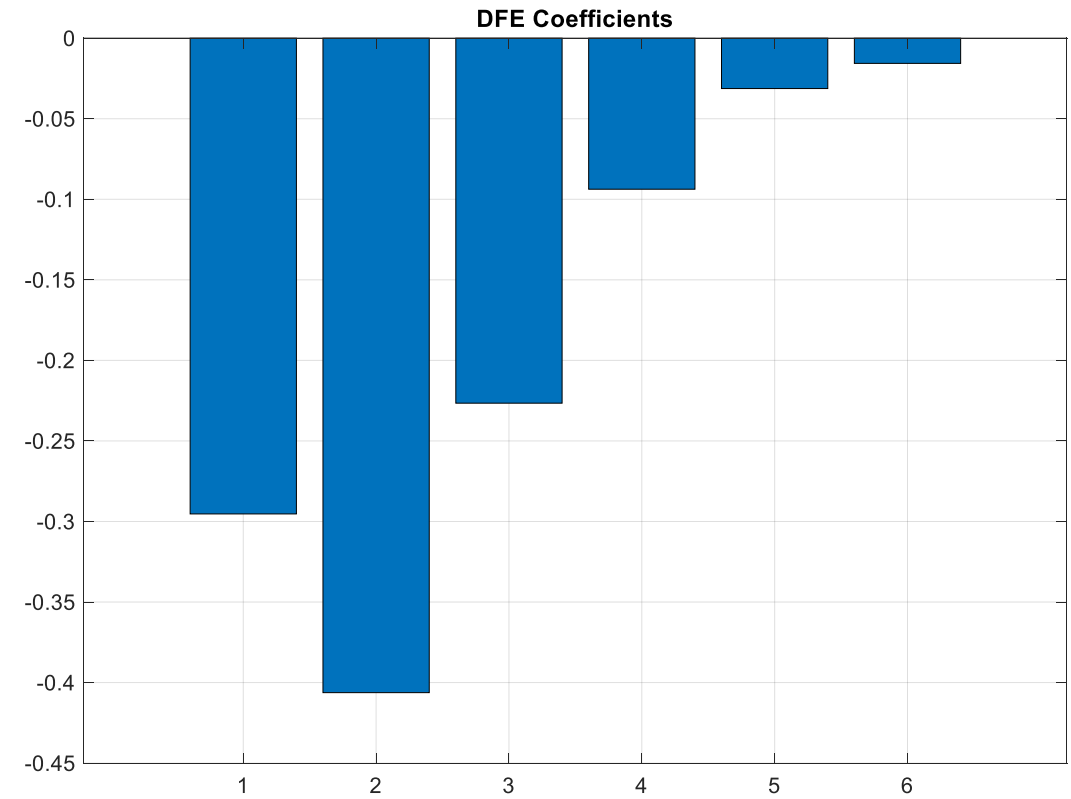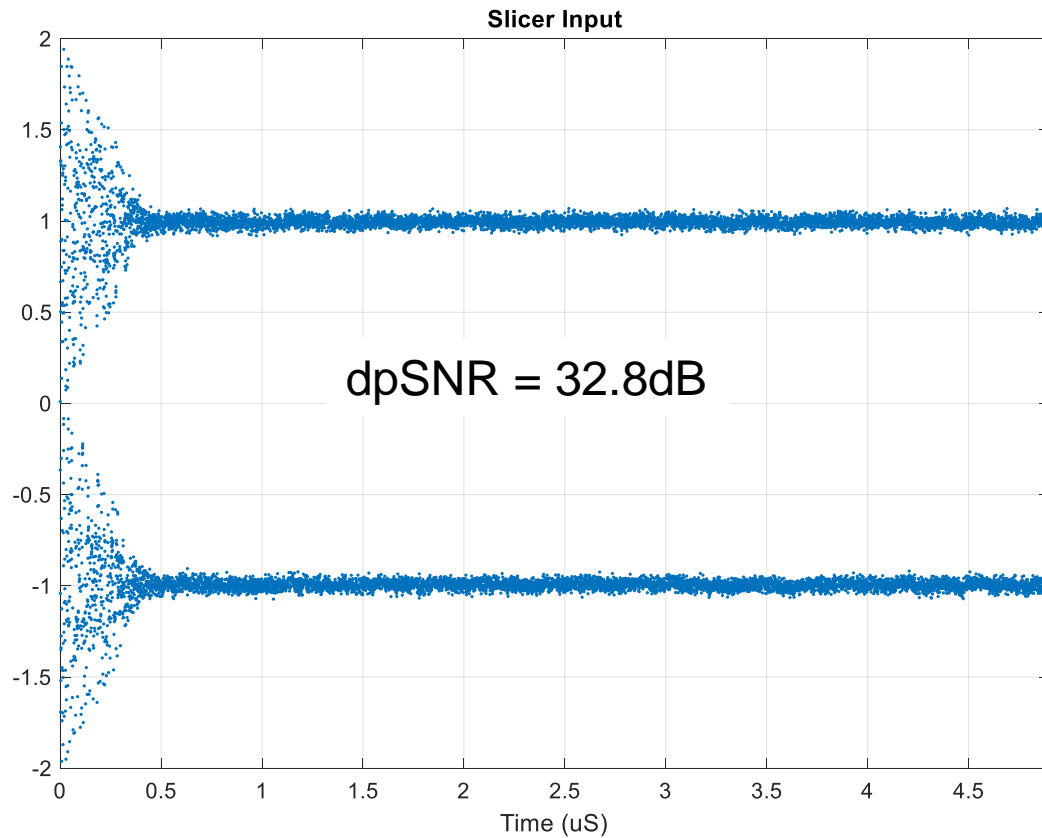
# Simulation results: Link Segment of 10.2m




- The Link Segment is a concatenation of smaller cables:  $3\text{m}+0.6\text{m}+3\text{m}+0.6\text{m}+3\text{m}= 10.2\text{m}$
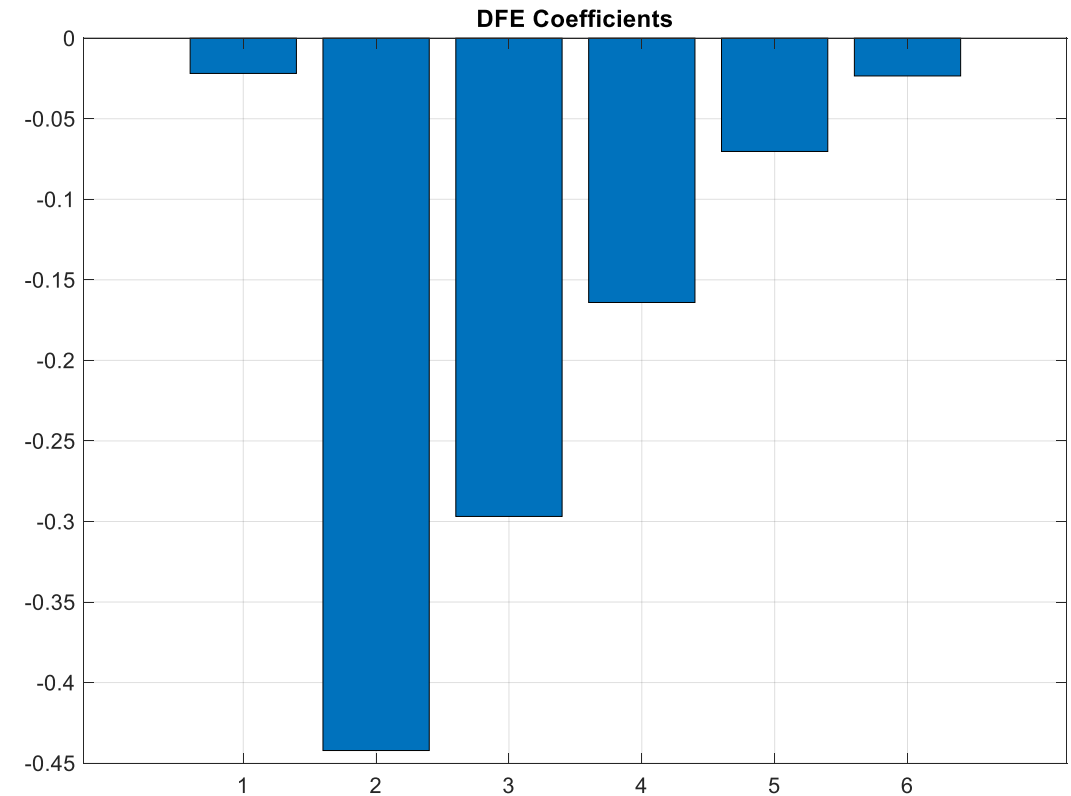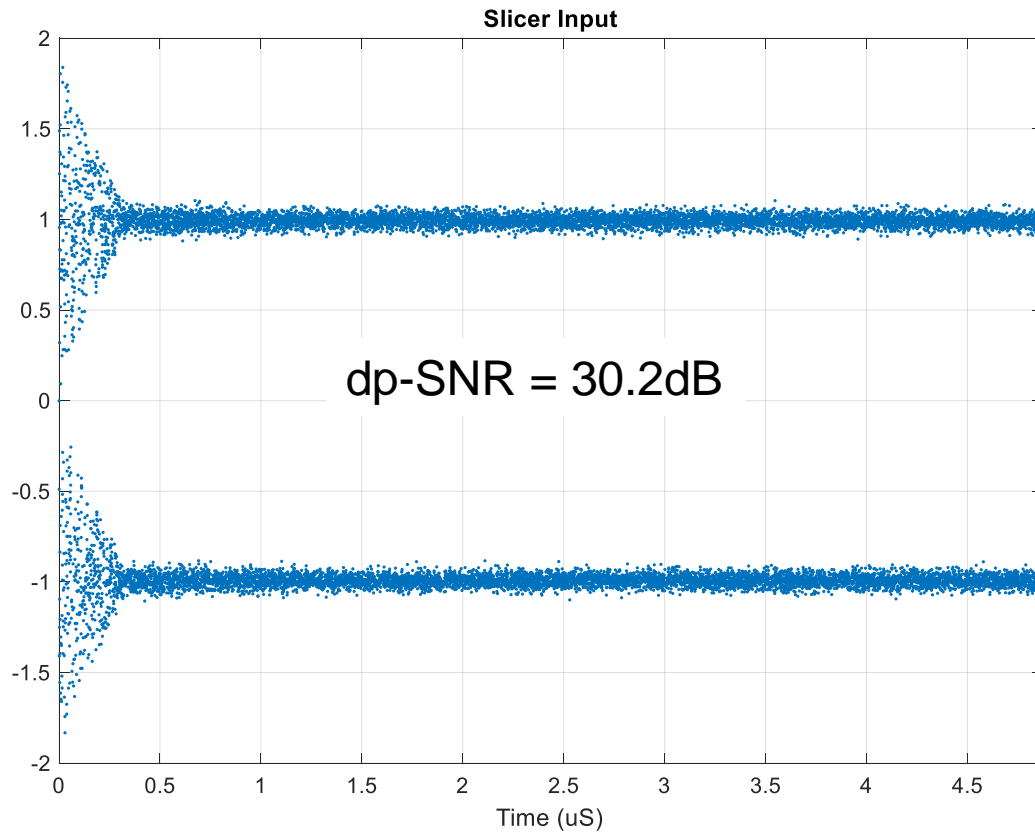
# Simulation results: Link Segment of 17.4m




- The Link Segment is a concatenation of smaller cables:  $3\text{m}+0.6\text{m}+3\text{m}+0.6\text{m}+3\text{m}+0.6\text{m}+3\text{m}+0.6\text{m}+3\text{m} = 17.4\text{m}$
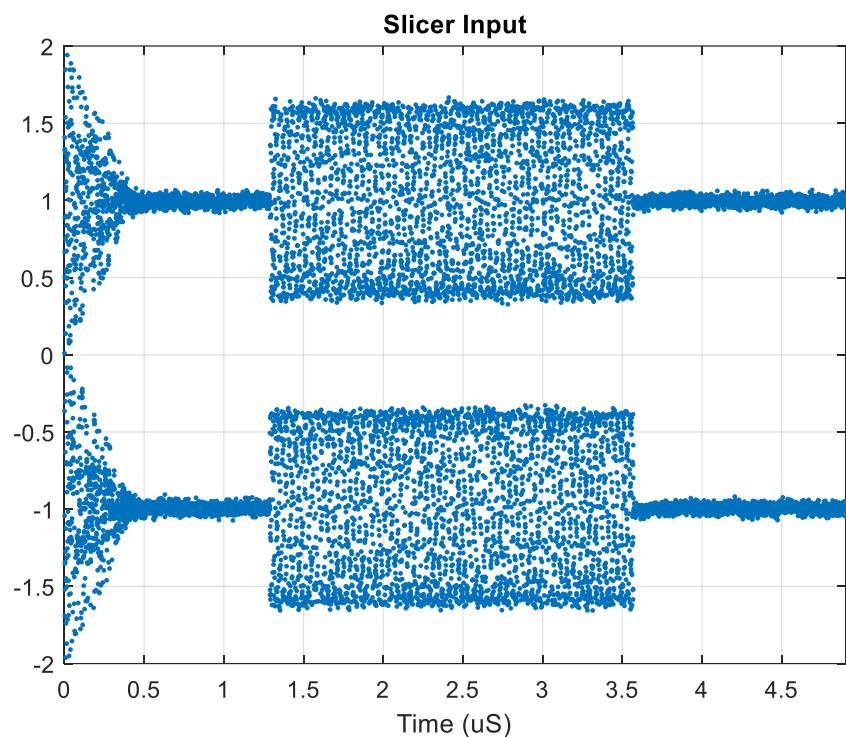
## Ingress noise effect, Link Segment of 10.2m



100mVpp Ingress noise at 425MHz

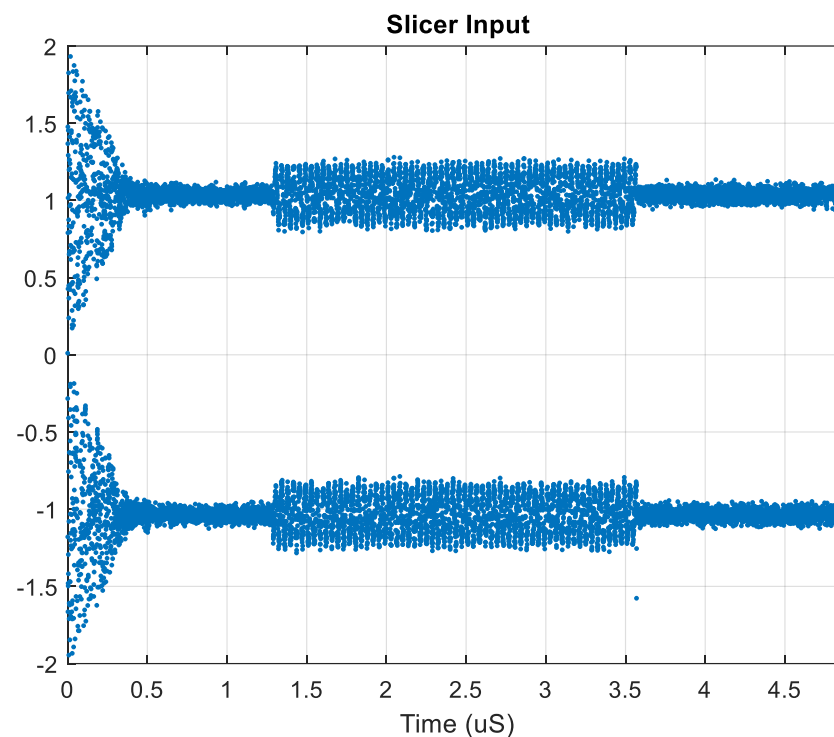


400mVpp Ingress noise at 27MHz

- CTLE or passive filter attenuates low frequency noises, therefore larger ingress noise levels are tolerated.



# Receiver Area and Power Estimation

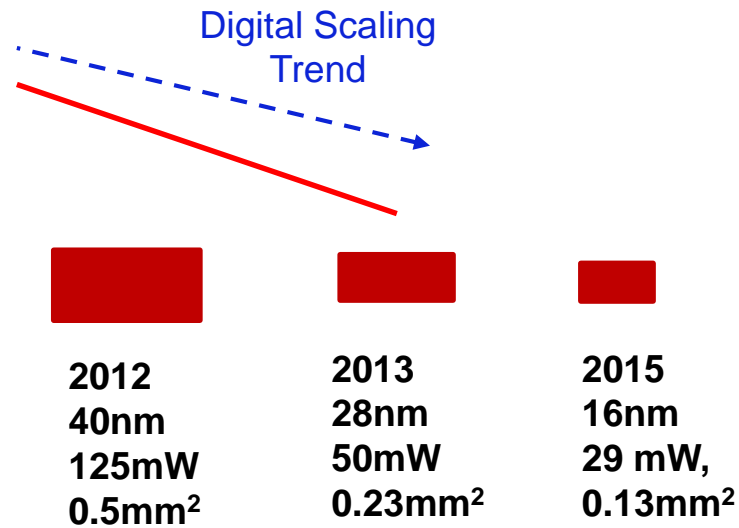


**Reference:** “Evolution of Multi-Gigabit Wireline Transceivers in CMOS”, Ichiro Fujimori, IEEE CSICS, 2014

- The plot shown on the left shows area and power for a 10Gbps SerDes transceiver evolution and it is referenced from CSICS 2014 paper.
- For 16nm technology, the numbers are estimated using digital scaling.
- The red line shows improved design practice beyond technology node size which could be used to build lower area and power transceivers even for larger technology nodes.
- Transceiver has three major blocks, TX, PLL and RX. RX side area and power is estimated to be about 50% of total area and power.
- For a 3Gsps receiver, only some portions of the receiver design is expected to scale down compared to a 10Gbps receiver. With that, the receiver power is expected to be below 10mW for a 16nm technology process and below 17mW for a 28nm technology. That is if it runs at 3Gsps continuously.
- For a TDD receiver with about 6% duty cycle, the power control mechanisms may be used to bring the average power to a level unmatched with any other technology (< 2-3mW with 16nm silicon and scales up for larger technology nodes).

# Integration with Image Sensor

From Dr. Mario Heid, OMNIVISION, 09/14/2023  
 On requirements for Integration with Image sensors.

Parameter	Worst case	Improved
Tx location and shape	Corner block	Edge strip
Tx logic IP power	400mW	< 200mW 
Si thickness	150µm	> 200µm
Thermal design	w/o thermal via	w/ thermal via
Pixel ΔT	> 5°C	< 2°C

[https://www.ieee802.org/3/ISAAC/public/091423/2023-09-18\\_Automotive%20camera%20PHY%20requirements%20study\\_V2.3.pdf](https://www.ieee802.org/3/ISAAC/public/091423/2023-09-18_Automotive%20camera%20PHY%20requirements%20study_V2.3.pdf)


Estimated Power Consumption of TDD Transceiver

	3Gbps Receiver with TDD power control	3Gbps Receiver with no Power control	Transmitter and PLL
16nm	< 3 mW	< 10 mW	~15 mW
28nm	< 5.5 mW	< 17 mW	~26 mW
40nm	< 7.5mW	< 25 mW	~37.5 mW

- TDD-based camera transceiver meets the <200mW power requirements for <2C temperature change even for technology sizes larger than 16nm given TDD with very low power consumption in the receiver.
- Power levels estimated for 16nm technology and scaled up for 28nm and 40nm.

# Camera side TDD-PHY versus Incumbents

880mW @45fps  
742mW @36fps

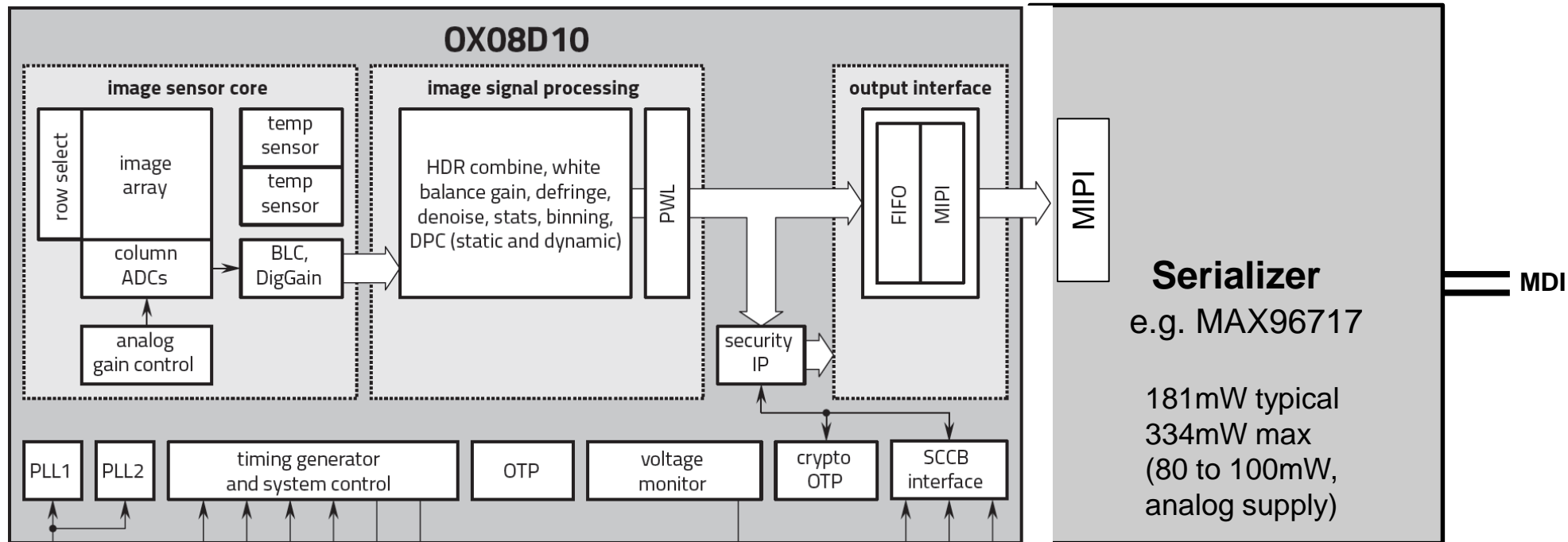

<https://www.ovt.com/products/ox08d10/>

[https://www.ieee802.org/3/dm/public/0724/Chini\\_Tazebay\\_3dm\\_01a\\_0724.pdf](https://www.ieee802.org/3/dm/public/0724/Chini_Tazebay_3dm_01a_0724.pdf)

- As a discrete serializer chip, TDD provides a competitive solution in cost and power by eliminating echo cancellation, small duty factor and low power PoC<sup>1</sup>.

1- [https://www.ieee802.org/3/dm/public/0924/Chini\\_Tazebay\\_3dm\\_01a\\_0924.pdf](https://www.ieee802.org/3/dm/public/0924/Chini_Tazebay_3dm_01a_0924.pdf)

# Summary

- An architecture of a 3Gbps equalizer is discussed which could be implemented in mixed mode technology and there is no need for unrolling of the DFE taps.
- The simulated performance of the link is provided when using a short, a medium and a long cable. In all cases, the decision point SNR of 30dB or more is achieved using low cost filtering techniques.
- The same receiver architecture may be used on both sides of a link operating at 2.5Gbps/100Mbps.
- The area and power of a 3Gbps SerDes transceiver and in particular, the camera side receiver is discussed. TDD-based PHY provides for extremely low power receiver design:
  - Very competitive with incumbent discrete solutions.
  - Well-suited for integration into image sensors.

Thank you for your attention

Questions?